

IV / SEM / ELECT / 2018(W) [24/05/2018, EX-REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Convert binary number $(110101.011)_2$ to decimal number. [2]
(b) Design 3 : 8 decoder with neat circuit diagram. [5]
(c) Which gates are referred to as universal gates and why? How other gates can be implemented by using NAND gates only? [7]
2. (a) Perform Excess-3 Subtraction of $97 - 72$. [2]
(b) Simplify the Boolean expression $Y(A, B, C) = A[B + C(\overline{AB + AC})]$. Also draw the logic circuit using NAND gates only. [5]
(c) Explain the working of Full adder. Draw its logic circuit and truth table. [7]
3. (a) Define modulus of a counter. [2]
(b) Explain the operation of 7 segments display. [5]
(c) Simplify the following expression using the k-map for 4 variable.
 $F(A,B,C,D) = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$ & implement this circuit by NAND gate. [7]
4. (a) What is an encoder and where it is used? [2]
(b) Differentiate between asynchronous and synchronous counters. [5]
(c) With neat diagram explain the operation of a clocked SR Flip flop with a functional table. [7]
5. (a) State associative and distributive law. [2]
(b) With a neat diagram explain the operation of PIPO and PISO shift register. [5]
(c) Explain the working of MOD – 10 binary counter with neat diagram. [7]
6. (a) Write the truth table of a NAND gat with symbol. [2]
(b) With a neat circuit diagram explain the function of **1: 8** DE-MUX. [5]
(c) Explain R-2R ladder type DAC with a neat diagram. [7]
7. (a) Which code is known as self correcting code and why? [2]
(b) Differentiate between combinational and sequential logic circuit. [5]
(c) Draw the logic diagram of Master-Slave JK Flip-Flop. Explain it with a functional table. [7]

-----☪-----☪----- ALL THE BEST -----☪-----☪----- ALL THE BEST -----☪-----☪-----

Collected By:-

Er. Paramananda Gouda
(Dept. of ETC, VCP Engg School)

IV/SEM/ELECT/2017(W) [17/05/2018, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Convert $(101011110.1011)_2$ to octal and hexadecimal numbers. [2]
 (b) Discuss 1: 4 De-multiplexer with circuit, truth table and implementation by gates. [5]
 (c) Which gates are referred to as universal gates and why? How other gates can be implemented by using one of these gates? [7]
2. (a) Define racing condition. How it can be avoided. [2]
 (b) Design an 8 : 3 encoder with neat circuit diagram. [5]
 (c) Show the logic diagram of clocked JK-Flip Flop. Explain its working with a functional table with a neat circuit diagram. [7]
3. (a) State De-Morgan's theorem. [2]
 (b) Simplify and minimize the 4-variable logic expression $F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$ by using k-map and implement its circuit by NAND gates only. [5]
 (c) Draw the logic circuit of full subtractor. Give its logic expression and truth table. Implement the logic circuit with any one of universal gates. [7]
4. (a) Define the term fan in, fan out and propagation delay. [2]
 (b) Explain the working of SISO, PISO shift register with the help of suitable logic diagram. [5]
 (c) Explain the working of a mod - 8 binary counter with neat diagram. [7]
5. (a) Find 2's complement subtraction of 10110-11010. [2]
 (b) Simplify the Boolean expression $Y = AB + A(B+C) + B(B+C)$.
 And draw the logic circuit for the simplified function. [5]
 (c) Design a magnitude comparator circuit. Whose outputs are $A > B$, $A = B$, $A < B$.
 Where A and B are 2 bit binary numbers. [7]
6. (a) Distinguish between combinational and sequential logic circuit. [2]
 (b) Explain weighted and non-weighted binary codes. [5]
 (c) Define SOP & POS term. Obtain canonical SOP & POS from the function $Y = A + B\bar{C}$. [7]
7. (a) Write the truth table of a Exclusive NOR gate. [2]
 (b) Explain the operation of seven segments display. [5]
 (c) Draw the diagram of D-Flip flop. Explain its working with functional table. [7]

IV/SEM/ELECT/2017(W) [28/12/2017, BACK]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

8. (a) Find the 1's complement and 2's complement of the binary 10110100. [2]
 (b) With a neat circuit diagram explain the function of 1: 4 Demultiplexer circuits. [5]
 (c) Which gates are referred to as universal gates and why? How other gates can be implemented by using NOR gates only? [7]
9. (a) Convert the decimal number $(95)_{10}$ into its equivalent BCD and Excess-3 Code. [2]
 (b) Explain the working of Half Adder. Draw its circuit using any one of Universal Gate. [5]
 (c) Obtain the minimal expression using k-map and draw the logic diagram using NAND gates Only. $F(P, Q, R, S) = \sum m(0, 1, 2, 7, 9, 12, 13) + \sum d(3, 5, 8, 10)$ [7]
10. (a) What is max term and min term? [2]
 (b) With neat logic diagram explain the operation of seven segment display. [5]
 (c) Design a magnitude comparator circuit. Whose outputs are $A > B$, $A = B$, $A < B$. Where A and B are 2 bit binary numbers. [7]
11. (a) Define fan in and fan out. [2]
 (b) Design a mod -5 synchronous counter with neat circuit diagram. [5]
 (c) With neat logic diagram explain the working of clocked JK-Flip Flop. Convert this flip flop into its equivalent D-flip flop and T-Flip Flop. [7]
12. (a) What is Racing and how it can be avoided? [2]
 (b) Differentiate between combinational and sequential logic circuit. [5]
 (c) Explain briefly about SISO, SIPO, PISO and PIPO Shift Registers. [7]
13. (a) Draw the block diagram of Full adder using two half adder and one OR gates. [2]
 (b) With neat sketch explain the working of Decimal to BCD Encoder. [5]
 (c) Design and explain the working of a 4 bit Ripple counter with neat logic diagram, truth table and timing diagram. [7]
14. (a) What is modulus of a counter? [2]
 (b) Design and explain the working of SR Flip flop using NAND gates with functional table. [5]
 (c) Explain the working of R-2R Ladder network type D/A converter with neat diagrams. [7]

IV/SEM/ELECT/2017(S) [APR-2017, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Which code is known as self correcting code and why? [2]
 (b) With a neat circuit diagram explain the function of 1 : 4 Demultiplexer. [5]
 (c) Design a 2bit Magnitude Comparator circuit whose outputs are $P > Q$, $P < Q$ and $P = Q$ Where P and Q are 2 bit nos. [7]
2. (a) Why multiplexers are referred to as data selector? [2]
 (b) Show the diagram of a clocked SR Flip-Flop. Explain its working with a functional table. [5]
 (c) Simplify and minimize the 4 variable logic express $F(P, Q, R, S) = \sum (0, 2, 4, 6, 8, 12, 15) + d(1, 3, 5, 7)$ by using K-map and implement this circuit by using NAND gate. [7]
3. (a) Define Racing Condition. How it can be avoided. [2]
 (b) Design a 4 : 2 Encoder circuit with a neat circuit diagram. [5]
 (c) Discuss the operation of an Asynchronous counter with its timing diagram. [7]
4. (a) State de Morgan's Theorem. [2]
 (b) Explain the working of SIPO and PIPO register with the help of a suitable logic diagram. [5]
 (c) Which gates are referred to as universal gates and why? How other gates can be Implemented by using any one of the universal gates? [7]
5. (a) Define modulus of a counter. [2]
 (b) Differentiate between combinational and sequential logic circuit. [5]
 (c) With a suitable logic diagram design a Decade Counter. Write its functional table too. [7]
6. (a) Why Demultiplexers are referred to as data distributors? [2]
 (b) Explain the operation of Full Subtractor. [5]
 (c) Draw the logic diagram of Master-Slave JK Flip-Flop. Explain it with a functional table. [7]
7. (a) Define Fan In and Fan Out. [2]
 (b) Simplify the Boolean expression, $y = \overline{(x \bar{y} z)(x \bar{y})} + yz$ and draw the logic circuit using NAND gates only. [5]
 (c) With a neat diagram explain the function of 4 : 1 Mux and 8 : 3 Encoder. [7]

ALL THE BEST

Collected By:-

*Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)*

IV/SEM/ELECT/2016(S) [APR-2016, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Define Racing Condition. [2]
 (b) Which gates are referred to as Universal Gates and Why? How other gates can be realized Using NAND Gates only. [5]
 (c) With neat circuit diagram explain the function of 1:4 De-Mux and 4:1 Mux. [7]
2. (a) Convert the decimal no. $(1000)_{10}$ into Binary. [2]
 (b) Design a 4:2 Encoder with neat circuit diagram. [5]
 (c) With neat sketch explain the working of PIPO and SIPO Shift Register. [7]
3. (a) Which code is known as self correcting code and why? [2]
 (b) A 7 bit hamming code coming out of transmission line is 0010100. If there any error? If Yes, in which data bit and what was the bit data actually transmitted. [5]
 (c) Draw the circuit diagram of clocked SR Flip-Flop. Explain it with a functional table. [7]
4. (a) Convert (10110101) from binary to gray code. [2]
 (b) Distinguish between combinational and sequential logic circuit. [5]
 (c) Design a 2 bit magnitude comparator circuit whose outputs are $P > Q$, $P = Q$ and $P < Q$, where P and Q are each two bit numbers. [7]
5. (a) Perform 2's complement subtraction of $1000011 - 1010111$. [2]
 (b) Explain the operation of seven segment display. [5]
 (c) Sketch logic diagram of clock JK flip – flop. Explain its working with a functional table. [7]
6. (a) Define the term Fan out and Resolution. [2]
 (b) Describe the operation of full subtractor with the help of truth table and circuit diagram. [5]
 (c) Explain the working of 4 bit ripple counter with truth table and timing diagram. [7]
7. (a) What is the difference between weighted and non-weighted binary code. [2]
 (b) Simplify the Boolean expression:

$$a[b + c(\overline{ab + ac})]$$
 Also draw the logic circuit using NAND gates only. [5]
 (c) Simplify the given expression using Karnaugh's Map and draw the logic circuit. Using NAND gate only. $F(a, b, c, d) = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$ [7]

ALL THE BEST

Collected By:-

*Er. Paramananda Gouda
 (Dept. of ETC, UCP Engg School)*

IV/SEM/ELECT/2015(S) [APR-2015, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**


 

 
 

Full Marks: 70

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) Convert the binary number $(10110111 . 1101)_2$ to decimal equivalent. [2]
 (b) What are the difference between 1's complement and 2's complement? Subtract $(39)_{10}$ and $(25)_{10}$ using 2's complement method. [5]
 (c) Explain ASCII code & its application & distinguish between weight and non-weight code. [7]
2. (a) What are the application of Gray code? [2]
 (b) Draw the symbol, truth table and expression for X – OR and AND gates. [5]
 (c) What is universal gate? Explain with examples and realize other gate. [7]
3. (a) Define De Morgan's law. [2]
 (b) Simplify the expression $Y = \overline{(AB + \bar{C})(A + B + C)}$ [5]
 (c) Define SOP and POS term. Obtain the canonical SOP form of the function $Y(A, B, C) = A + \bar{B}\bar{C}$ and draw the truth table. [7]
4. (a) What is parity bit? [2]
 (b) Simplify the following expression using the K-map for four variables. $Y(A, B, C, D) = \sum(1,5, 10, 11, 12, 13, 15) + d(14, 9)$ and implement using AOI gates. [5]
 (c) Design a Full adder circuit and implement using NAND gates. [7]
5. (a) What are the different between CLC and SLC circuits (any two)? [2]
 (b) Explain the working of 2 bit magnitude comparator with logic expression and gate level circuits. [5]
 (c) Discuss (1.4) Demultiplexer with logic circuit, truth table and implementation by gates. [7]
6. (a) Define fan – in and fan – out. [2]
 (b) Define flip-flop and explain clock JK flip-flop using NAND gates only. [5]
 (c) Explain the working of 4 bit ripple counter with truth table and timing diagram. [7]
7. (a) What is racing condition and how it is avoided? [2]
 (b) Explain the working of different types of shift registers. [5]
 (c) Explain R – 2R ladder type DAC with a neat diagram. [7]
8. (a) Define Resolution and conversation time. [2]
 (b) Explain Ramp type ADC with neat circuit diagram. [5]
 (c) Explain LED driver Using IC 7447 decoder. [7]

--------------- **ALL THE BEST** --------------- **ALL THE BEST** ---------------

Collected By:-

*Er. Paramananda Gouda
 (Dept. of ETC, VCP Engg School)*

IV/SEM/ELECT/2014(S) [APR-2014, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions

The figures in the right-hand margin indicate marks

1. (a) State De Morgan's Theorem. [2]
 (b) Design a 2 bit magnitude comparator circuit whose outputs are $A > B$, $A = B$, $A < B$, Where A and B are 2 bit numbers. [6]
 (c) Define the term offset voltage of D/A converter. Explain the working of weighted resistor type DAC converter with a neat block diagram. [8]
2. (a) Find the 2's complement subtraction of $100011 - 1010111$. [2]
 (b) Which code is known as self correction code and why? A 7 bit hamming code coming out of transmission line is 0010100. Is there any error? If yes, in which data bit and what was the 4 bit data actually transmitted? [6]
 (c) Simplify the expression using K-Map
 $F(A, B, C, D) = \sum m(4, 7, 12, 15) + d(0, 1, 2, 3, 8, 9, 10, 11)$ & implement it with NAND gate. [8]
3. (a) Define Modulus of a counter? [2]
 (b) Differentiate between Asynchronous and Synchronous counters? [6]
 (c) Draw and write down the function table for the conversion of [8]
 (i) SR to JK FF (ii) T to JK FF (iii) SR to D FF (iv) JK to T FF
4. (a) Write down the truth table of a 2input Exclusive OR gate? [2]
 (b) Show logic diagram of a clocked JK flip-flop. Explain its working with a functional table? [6]
 (c) Which gates are referred to as universal gates and why? How other gates can be implemented by using universal gates. [8]
5. (a) What do you mean by Fan In, Fan out and propagation delay? [2]
 (b) Explain with sketch the working of a 2 input TTL NAND gate? [6]
 (c) Draw the logic circuit of full subtractor. Give its logic expression and truth table. Implement the logic circuit with any one of universal gates? [8]
6. (a) What is an encoder and where it is used? [2]
 (b) With a neat diagram explain the operation of PISO Register? [5]
 (c) Design a synchronous 4 bit up down counter using D flip-flops? [7]
7. (a) What is racing condition? [2]
 (b) Explain the operation of seven segment display and LED? [5]
 (c) Design a combinational logic circuit converting 4 bit binary to decimal decoder circuit. [7]

----- ALL THE BEST -----

Collected By:-

*Er. Paramananda Gouda
 (Dept. of ETC, UCP Engg School)*

IV/SEM/ELECT/2013(S) [APR-2013, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2
The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
- (a) What is the base or radix of a number system?
 - (b) Convert $FADE_{16}$ to Binary and Octal.
 - (c) Convert 7743_g to Binary and Hexadecimal.
 - (d) Draw the IC pin configuration of NOR gate and IC number.
 - (e) What is the basic difference between combinational and sequential logic circuit.
 - (f) What is parity of a binary number?
 - (g) What are the floating inputs and why they are not allowed?
 - (h) Define FANIN and FAN out.
 - (i) Name different IC families and which is fastest family.
 - (j) What is the difference between RAM and ROM?
2. Answer any **FIVE** question: [5x6]
- (a) State and prove Demorgan's theorem. Explain with relevant diagrams, Boolean expressions and functional tables.
 - (b) What are all the Universal logic gates? Why are they called so? Explain with relevant logic diagrams, Boolean expressions.
 - (c) Explain the working of a full adder circuit.
 - (d) Explain the working of a clocked RS flip flop using NAND gates. Why the set and reset inputs are known as asynchronous input signals?
 - (e) Explain the working of 4 bit SISO register with a neat diagram and timing diagram.
 - (f) Explain the working of a 4 bit binary asynchronous counter with circuit and timing diagrams.
 - (g) Explain the terms RAM, ROM, PROM, EPROM and EEPROM.
 - (h) How the defence application ISs are different from the ICs used in common applications.
3. Explain the working of a 4 bit binary adder subtractor circuit, with neat circuit. [10]
4. Explain the working of a 16:1 multiplexer. [10]
5. Simplify $f(A, B, C, D) = \sum m(0, 1, 2, 5, 6, 8)$ & $d(3, 4, 7, 14)$ using map & draw logic circuit. [10]
6. Explain the working of a synchronous type. Decade counter with neat sketch. [10]
7. Explain the working of a successive approximation type A/D converter. [10]

ALL THE BEST

ALL THE BEST

Collected By:-

Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)

IV/SEM/ELECT/2012(S) [APR-2012, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2
The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
 - (a) What do you mean by radix of a number system?
 - (b) Why complementary numbers are used?
 - (c) State De Morgan's Theorem.
 - (d) Draw the output waveform of the given logic circuit.
 - (e) What is the meaning of Min. term and Max. term?
 - (f) Define demultiplexure and its use.
 - (g) What is flip-flop and where it is used?
 - (h) Explain the term 'Fan-in and Fan-out'.
 - (i) What is the percentage resolution of a 8-bit DAC?
 - (j) Draw the AOI logic circuit of $Y = \bar{A}.B + \bar{C}.A$.
2. Answer the following in brief (any five): [5x6]
 - (a) Which gates are called universal gates and how other gates can be realized?
 - (b) Explain the working of a clocked RS flip-flop using NAND logic circuit.
 - (c) Simplify Boolean expression $X = \overline{PQ} + \overline{PR} + \overline{PQ}.R$ & draw logic circuit using NOR gate only.
 - (d) Distinguish between combinational logic and sequential logic.
 - (e) Design a 4:1 multiplexer with neat circuit diagram.
 - (f) What is the necessity of digital code? Differentiate between weighted code and non-weighted code. How Gray code is used to convert to binary?
 - (g) Define a half adder. How a full adder can be constructed using half adder? Draw the logic circuit and truth table of full adder.
 - (h) Explain the operation of seven segment display.
 - (i) With neat circuit diagram, explain the working of 4-bit ripple counter.
3. Simplify the minimal minterm expression of $f(W, X, Y, Z) = \sum m(0, 1, 2, 5, 6, 8) + d(3, 4, 7, 14)$ using Karnaugh map & draw logic circuit using NAND gate only.
4. Explain the working of JK flip-flop and draw its truth table. How JK flip-flop can be constructed into (i) T-flip-flop, (ii) D-flip-flop.
5. Explain working of a Mod-10 binary counter with neat diagram & show its timing diagram. [10]
6. Explain with a sketch the successive approximation A/D converter. [10]
7. Write short notes on any two of the following: [5x2]
 - (a) Explain the working of SIPO shift register.
 - (b) One-bit comparator circuit.
 - (c) Racing condition and how it can be avoided.

IV/SEM/ELECT/2011(S) [APR-2011, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2
The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
 - (a) What is the base of a number system?
 - (b) Convert $(111101000.0111)_2$ to octal and hexadecimal numbers.
 - (c) Find the two's complement of a number $(1000000)_2$.
 - (d) What is donot care condition?
 - (e) What is parity and how it is used?
 - (f) What do you mean by latching?
 - (g) Define modulus of a counter.
 - (h) Explain the meaning of 'Fan-in' and 'Fan-out' with reference to logic families.
 - (i) What is Demultiplexer?
 - (j) What will be the resolution of 16 bits D/A converter?

2. Answer any six: [2x10]
 - (a) What is Universal gate and how the other gates can be implemented by using any one of the Universal gate?
 - (b) With neat circuit diagram explain the function of 1:4 Demultiplexer circuit.
 - (c) Show the logic diagram of a clocked RS flip-flop based on NAND gates. Explain its working with a functional table.
 - (d) Explain the basic operation of a shift register with neat diagram.
 - (e) What is self correcting code? Explain the format for self correcting code.
 - (f) Differentiate between combinational logic and sequential logic.
 - (g) Explain the working of a Ladder Network type D/A converter with diagram.
 - (h) Simplify the Boolean expression $F = XY + XYZ + XY\bar{Z} + \bar{X}YZ$ using Boolean algebra and draw the logic circuit.

3. Simplify the minimal SOP and POS expressions $F(A, B, C, D) = \sum(3,4,6,7,11,12,13,14)$ [10]
4. Design a 2-bit digital comparator circuit for comparing two-2bit numbers A and B. [10]
5. Explain the working of 4-bit ripple counter with truth table and timing diagram. [10]
6. What is Racing? How it is eliminated in M/S JK flip-flop? Explain with suitable diagram. How the JK flip-flop is converted into 'D' and 'T' type flip-flop?
7. Write short notes on any two: [5+5]
 - (a) Seven segment display
 - (b) Compare between LED and LCD
 - (c) Full subtractor.

IV/SEM/ELECT/2010(S) [APR-2010, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2

The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
 - (a) What do you mean by ‘Radix’ of a number system?
 - (b) Write the truth table of a AND gate with symbol.
 - (c) What is Hollerith code and why it is essential?
 - (d) Draw the K-map of a maxterm expression fro which is represented as

$$F(A, B, C) = (A + B) (B + C) (C + A)$$
 - (e) What do you mean by Fan-In and Fan-Out?
 - (f) Define modulus of a counter and why it is essential.
 - (g) Define NOR Latch.
 - (h) Use 2’s complement subtract 11101-1101.

2. Answer any six: [2x10]
 - (a) If two inputs A and B having 10101 and 11100 data are applied to the NAND gate inputs, serially determine the output waveform of NAND gate with truth table.
 - (b) Minimize the following Boolean function using K-map and implement in any one of the universal gates: $F(A, B, C, D) = \sum m(5,7,8,10,13,15) + \sum d(0,1,2,3)$
 - (c) Design a decimal decoder circuit using gates.
 - (d) Explain the operation of TTL – NAND gate with a neat circuit diagram.
 - (e) Explain briefly operation of BCD seven segment decoder.
 - (f) What is ripple counter and compare between synchronous and ripple counter?
 - (g) Design a combinational circuit having three input whose output is equal to 1 if the input variables have more 1’s than 0’s. the output is 0 otherwise.

3. Given the Boolean algebra function $F = xy + x’y’ + y’z$ [10]
 - (a) Implement it with AND, OR and inverter gates.
 - (b) Implement it with NAND gate only.
 - (c) Implement it with NOR gate only.
 - (d) Give its truth table.

4. Explain working of full subtractor with a neat diagram & implement using universal gates. [10]
5. Define clocked JK flip-flop and explain working of JK flip-flop using NAND-NAND and AND-OR with truth table. [10]
6. What is shift register and what are its classification and explain the operation of serial shift-register with neat circuit diagram? [10]
7. Write the short notes on any two: [5+5]
 - (a) Error detection and correction code
 - (b) Multiplier
 - (c) ECL logic.

IV/SEM/ELECT/2009(S) [APR-2009, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2
The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
 - (a) Subtract 0111_2 from 1010_2 .
 - (b) Multiply 1010_2 by 101_2 .
 - (c) Convert the decimal number 268_{10} into hexadecimal and octal number system.
 - (d) Draw the truth for NAND gate and construct the same using AND and NOT gate.
 - (e) What is weight code? Where is it used?
 - (f) Draw the truth table for D-flip-flop and give the symbol of D-flip-flop.
 - (g) What are the application of full adder circuit?
 - (h) A 16×8 ROM stores the words in its first two location i.e. $R_0 = 1011\ 1111$, $R_1 = 0011\ 1100$.
Express the store contents in decimal and hexadecimal.
 - (i) Where shift registers are used?
2. Answer any **SIX**: [2x10]
 - (a) Design a half adder circuit and implement using NAND gate only.
 - (b) Writs the function of a clocked JK flip-flop with truth table and necessary circuit diagram.
 - (c) What are the different characteristics of Digital logic Families?
 - (d) Explain briefly working of Seven Segment Decoder with a neat circuit diagram.
 - (e) Mention the difference between weighted and un-weighted codes with suitable examples.
Give application of ASCII code.
 - (f) State and prove De Morgan's theorems with relevant logic diagrams and Boolean's expressions.
3. Explain working of 4 bit synchronous counter. How it can be converted to a decade counter?[10]
4. (a) Draw AND – OR logic circuit for the expression $(A + B)(C + D)(E + F)$ and change this to NOR logic.
(b) Explain briefly DTL logic of NAND gates with a neat circuit diagram.
5. Simplify the expression using K-map $F(A, B, C, D) = \sum(1,5,7,8,9,10,11,14,15)$ and implement using NAND gates only. [10]
6. What are different types of shift registers and explain them with a neat circuit diagram. [10]

ALL THE BEST

ALL THE BEST

Collected By:-

Er. Paramananda Gouda
(Dept. of ETC, UCP Engg School)

IV/SEM/ELECT/2008(S) [APR-2008, REG]

DIGITAL ELECTRONICS

Sub Code – **ETT-421**

Full Marks: 80

Time: 3 Hours

Answer any **FIVE** Questions including Q. nos 1 & 2
The figures in the right-hand margin indicate marks

1. Answer **ALL** question: [2x10]
 - (a) Multiply $(1001.11)_2 \times (100.11)_2$.
 - (b) Convert $(A268.12)_{16}$ to Binary and Decimal.
 - (c) Draw the diode circuit for AND gate.
 - (d) Draw the truth-table and symbol for NAND gate.
 - (e) What is D Latch?
 - (f) What are the families of ICs that are widely in use? Which is the fastest of them?
 - (g) What do you mean by modulus of counter?
 - (h) What is 7-bit code and whether it is weighted or non-weighted?
2. Answer any six: [2x10]
 - (a) Why NAND and NOR gates are called universal gate? Justify your answer.
 - (b) Realize EX – OR gate using minimum no of NAND gate & give truth table for EX-OR gate.
 - (c) State and prove de Morgan's theorem.
 - (d) Explain the working of a Half Adder using NAND gate only.
 - (e) Draw a 4-bit ripple counter and explain its working.
 - (f) What is flip-flop? Explain the working of a clocked JK flip-flop.
 - (g) An AND gate is followed by a NOT gate. With inputs A and B, obtain the Boolean expression of the output C. Draw its truth table.
3. (a) Simplify the following Boolean function is product of sums: [6]
 $F(A, B, C, D) = \sum(0, 1, 2, 5, 8, 9, 10)$
 - (b) What is the simplified sum of product form of F?
4. (a) Draw the internal circuit configuration of a TTL NAND gate. [5]
 - (b) Using Boolean algebra, write an expression for output Y of circuit. Hence identify the circuit
5. Explain the working of a decade counter and draw its timing diagram. [10]
6. Write short notes on any two of the following [5 x 2]
 - (a) Shift register
 - (b) Full adder circuit
 - (c) Working of decoder

ALL THE BEST

ALL THE BEST

Collected By:-

Er. Paramananda Gouda
(Dept. of ETC, VCP Engg School)

UCP Engineering School

Fb/Discover Brahmapur

